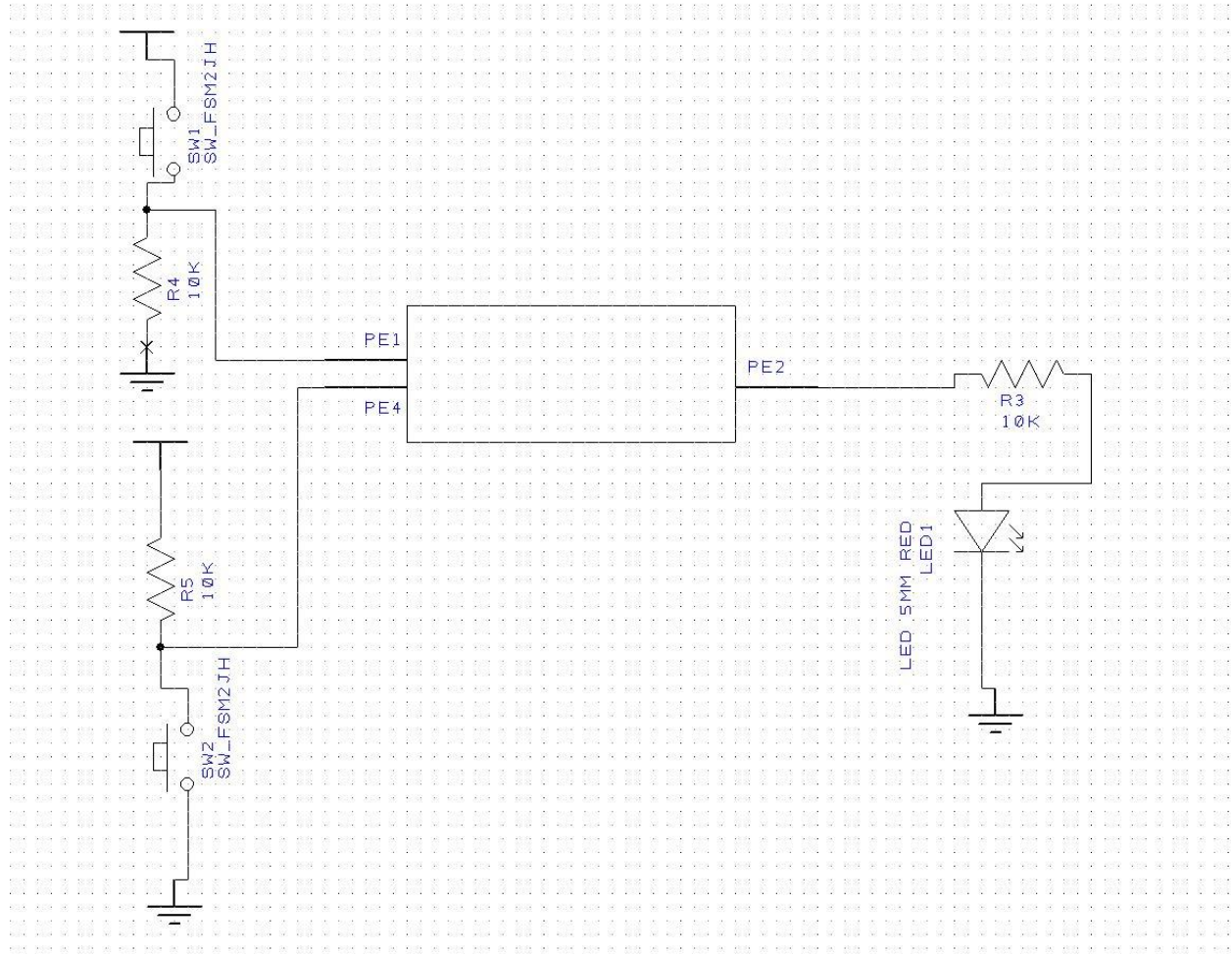


Ayan Basu
EID: ab73287
Dr. Yerraballi - Unique #17070
16 February 2021

Lab 3 Deliverables

PART A - Circuit Diagram




PART B - Estimated LED Voltage & Current

Estimated Voltage Value (Vd): $V_d = 1.600170231$ Volts

Estimated Current Value (Id): $I_d = 3.4046175$ Amperes

$R=470$, find I_d & V_d ; \rightarrow Ohm's Law: $V_d = I_d \cdot R$; $V_d = 470 I_d \rightarrow$ given equation in Lab Manual,
 $I_d = 20 \cdot V_d - 32$; $I_d = 20 \cdot (470 I_d) - 32 \rightarrow I_d = 0.0034046175$ Amps $\rightarrow I_d = 3.4046175$ mAmps \rightarrow
 $V_d = I_d \cdot R \rightarrow V_d = 3.4 \cdot 470 \rightarrow V_d = 1.600170231$ Volts

PART C - Debugging Screenshot

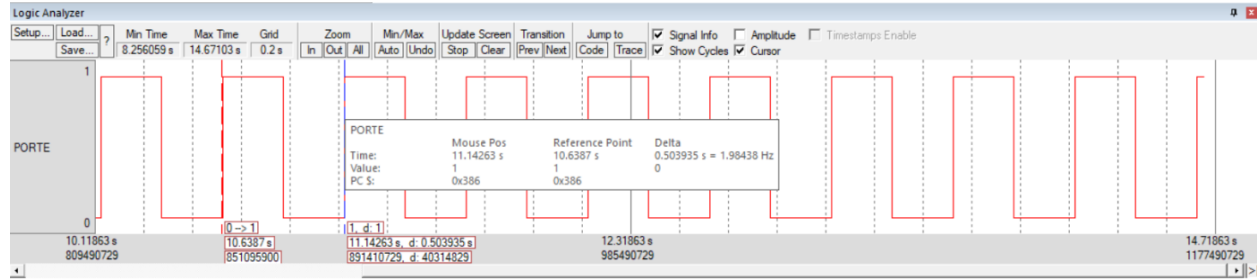

PART D - Switch Measurements

Parameter	Value	Units	Conditions
Resistance of the 10kΩ resistor, R1	10000	ohms	with power off and disconnected from circuit (measured with ohmmeter)
Supply Voltage, $V_{+3.3}$	3.28	volts	Powered (measured with voltmeter)
Input Voltage, V_{PE1}	0	volts	Powered, but with switch not pressed (measured with voltmeter)
Resistor current	0	mA	Powered, but switch not pressed $I = V_{PE1}/R1$ (calculated and measured with an ammeter)
Input Voltage, V_{PE1}	3.28	volts	Powered and with switch pressed (measured with voltmeter)
			Powered and switch pressed

Resistor current	0.000328	mA	$I = V_{PE1}/R1$ (calculated and measured with an ammeter)
------------------	----------	----	--

PART E - LED Measurements

Row	Parameter	Value	Units	Conditions
1	Resistance of the 470Ω resistor, R19	470	ohms	with power off and disconnected from circuit (measured with ohmmeter)
3	TM4C123 Output, V_{PE2} input to 470Ω	0	volts	with PE2 = 0 (measured with voltmeter relative to ground). We call this V_{OL} of the TM4C123.
4	LED a+, V_{a+} Bottom side of R19 (anode side of LED)	0	volts	with PE2 = 0 (measured with voltmeter relative to ground). This measurement is also weird, because it too is floating.
5	LED voltage	1.6	volts	calculated as $V_{a+} - V_{k-}$ (V_{k-} is ground).
6	LED current (off)	0	mA	calculated as $(V_{OL} - V_{a+})/R19$
7	TM4C123 Output, V_{PE2} input to 470Ω	2.9	volts	with PE2 = 1 (measured with voltmeter relative to ground). We call this V_{OH} of the TM4C123. We

				previously assumed this was 3.2V.
8	LED a^+ , V_{a^+} Bottom side of R19 (anode side of LED)	2.8	volts	with PE2 = 1 (measured with voltmeter relative to ground)
9	LED voltage	1.62	volts	calculated as $V_{a^+} - V_k$ (V_k is ground).
10	LED current (on)	2.76	mA	calculated as $(V_{OH} - V_{a^+})/R19$
11	LED current (on)	5.03	mA	measured with an ammeter