
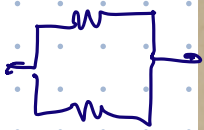


## Breadboard / Parallel vs series resistors

① parallel

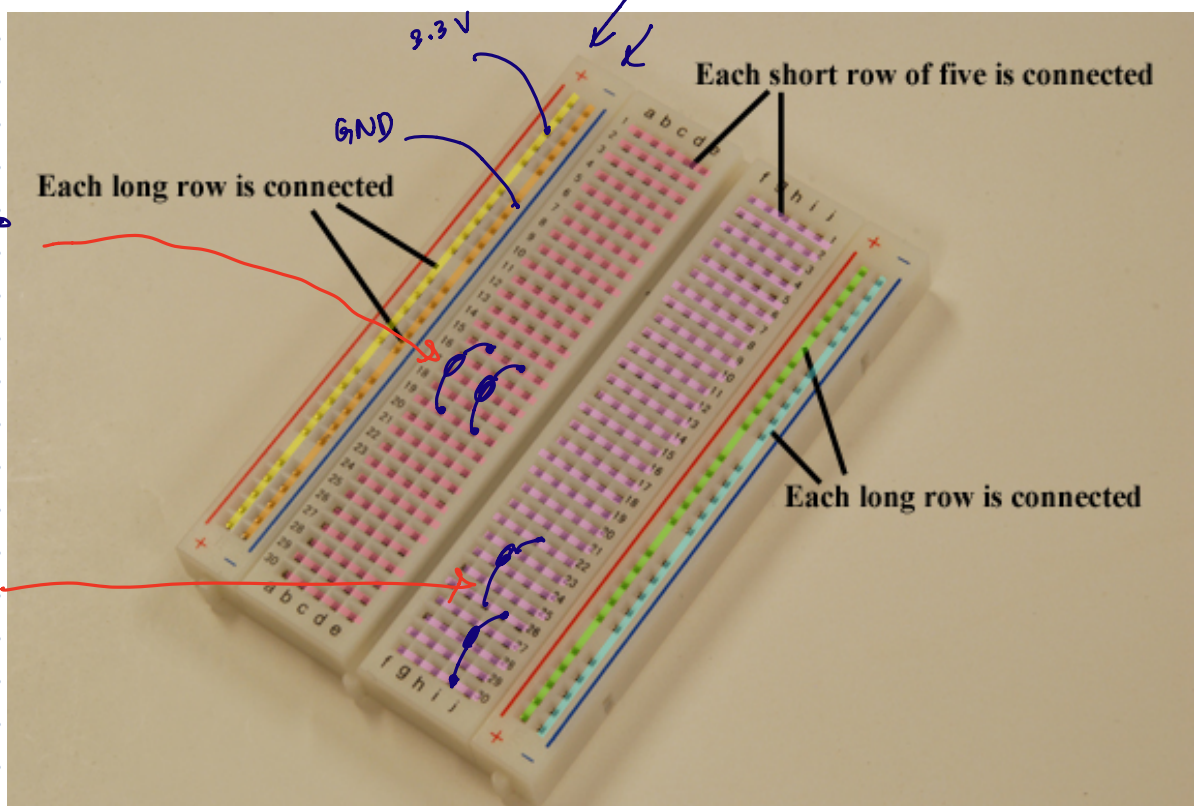


② Series



# LED

## ① Resistance calculation

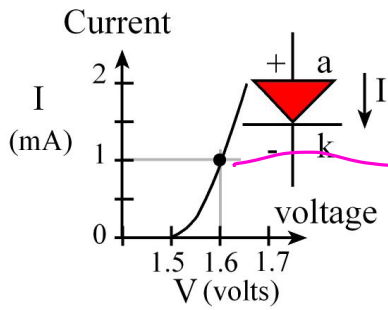



(a) LED curve

$(V_d, I_d)$


$V_d = 1.8V$

$I_d = 3mA$

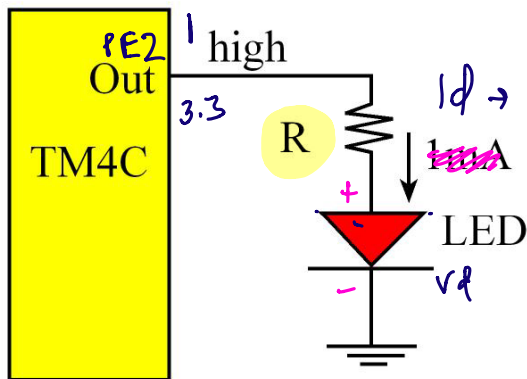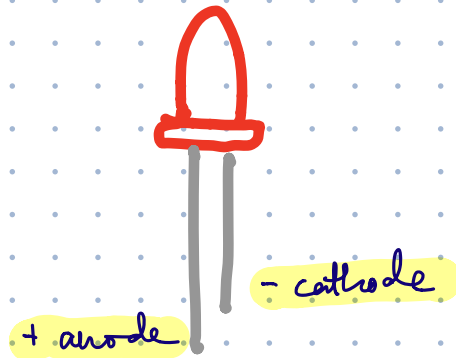Power =  $V I$   
 $\Rightarrow$  brightness



(b) Positive logic interface

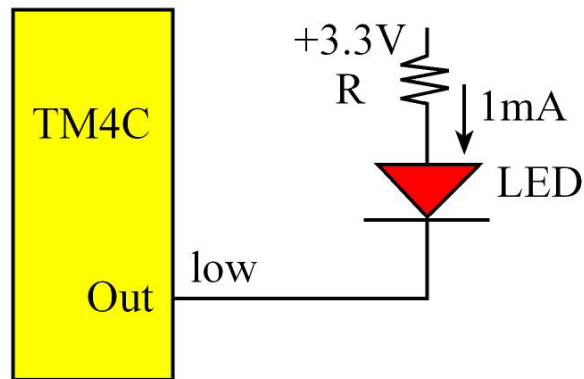

(c) Negative logic interface

$$\frac{D}{1} \quad \frac{A}{3.3V} \Rightarrow 3.3 - I_d R - V_d = 0$$


$$\Rightarrow R = \frac{3.3 - V_d}{I_d} = \frac{3.3 - 1.8}{3 \times 10^{-3}}$$

$$= 500 \Omega \approx 470 \Omega$$

$\nearrow 3mA$   $\nearrow 1.8$


$\hookrightarrow$  negligible  $V_d$  don't care

## ② Wiring an LED



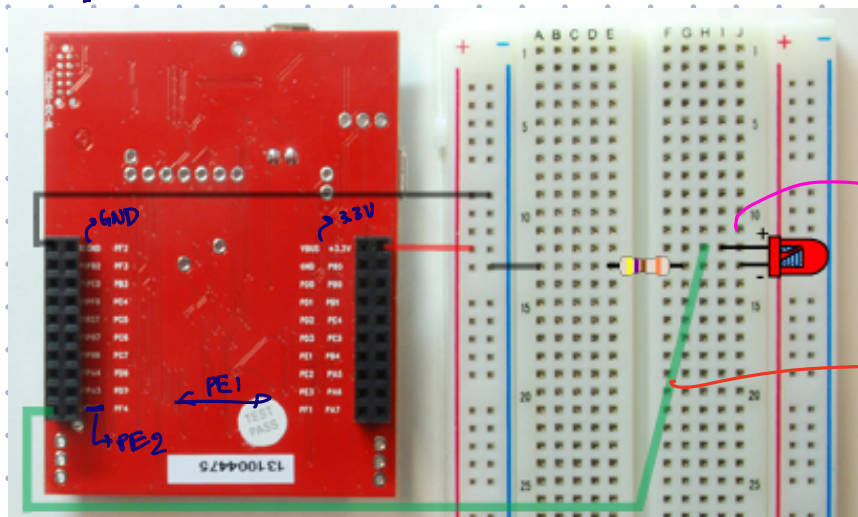


# Switch

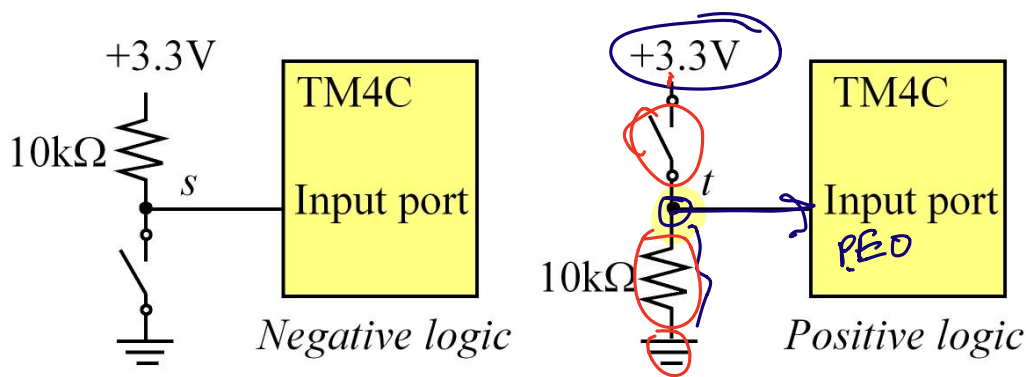
## ① Positive vs. negative logic switch diagrams



## ② Your switch

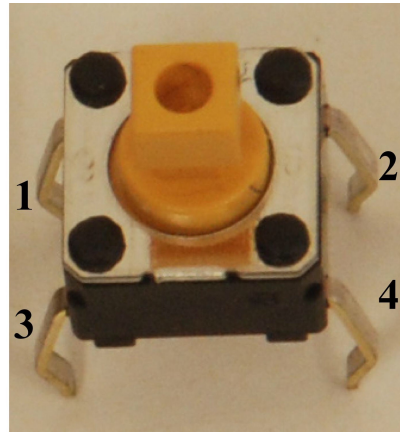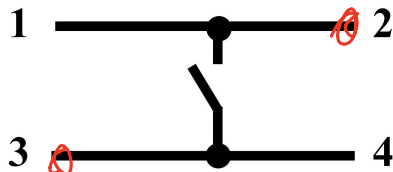
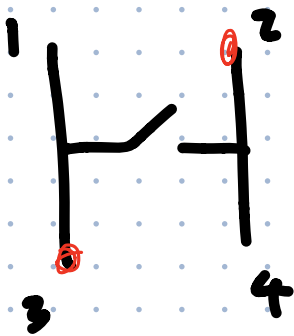

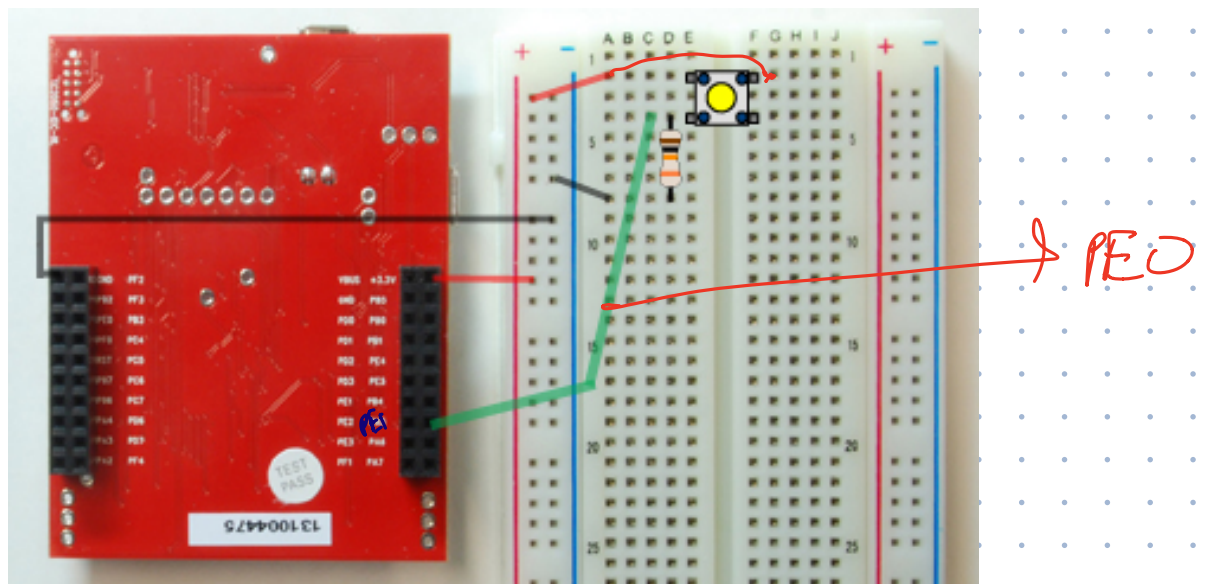
## ③ Wiring a switch → recommended → wire diagonally





# FINAL SETUP

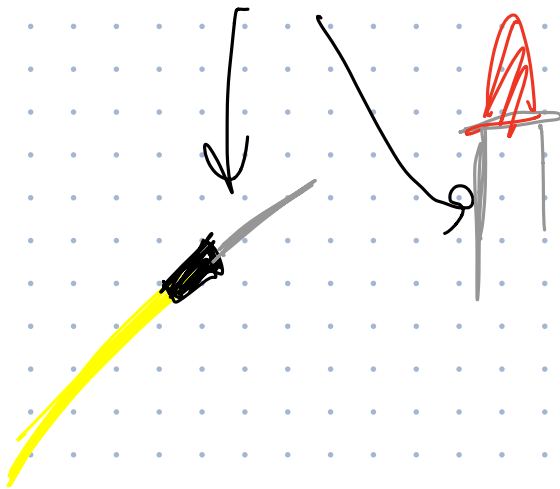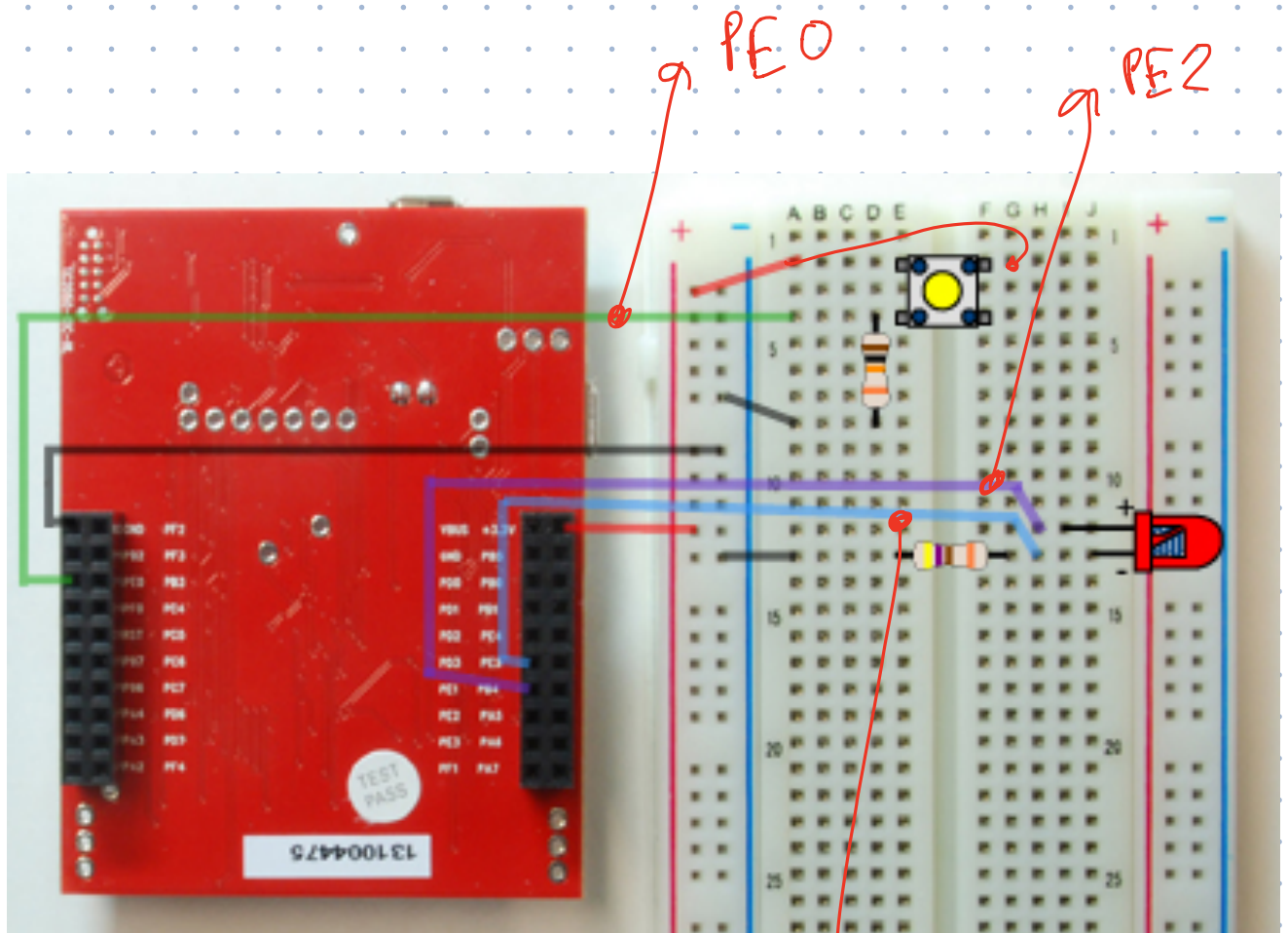

PD3, for checking  
with Texas Display

